

Switching in Full Adder

Consider the selection part of the previous circuit.

The outputs from the AND gates are always either $(x, 0)$ or $(0, y)$.

Then for the OR gate, if one input is 0, the output reflects the other input.

So the output from the OR gate is always either (x) or (y) , controlled by whether s (c_{in} in the other example) is 0 or 1.

If s is 0, output is x .

If s is 1, output is y .

This circuit is called a 2~1 line multiplexor (2~1 line MUX).

Where We're Going

Using multiplexors like this, we can create different circuits by connecting inputs to different outputs.

This will allow us to create different pathways/instructions in our machine.

How Would We Choose Between 4 Inputs?

Use a 4~1 line multiplexor.

This takes 4 inputs, has 2 selectors (since 2 bits means $2^2 = 4$ possible states), and one output.

These are I_0 to I_3 and S_1 to S_0 .

If $(S_1, S_0) = (0, 0)$ then I_0 is output

$(0, 1) \rightarrow I_1$

$(1, 0) \rightarrow I_2$

$(1, 1) \rightarrow I_3$

Note it's by design that the binary numbers input are 0 for I_0 up to 3 for I_3 .

For the 4~1 line MUX, you use a 4-input OR gate at the end, which is basically a cascading OR gate where you OR two inputs, then the result with the next input, and so on until finished.

The same can be done with an AND gate.