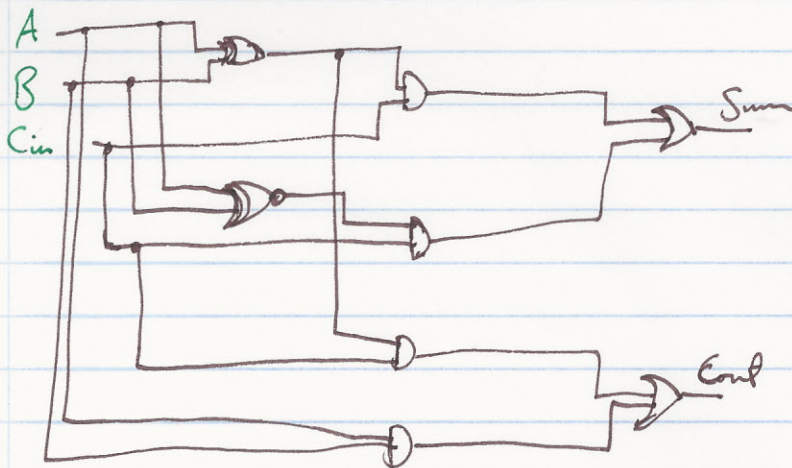
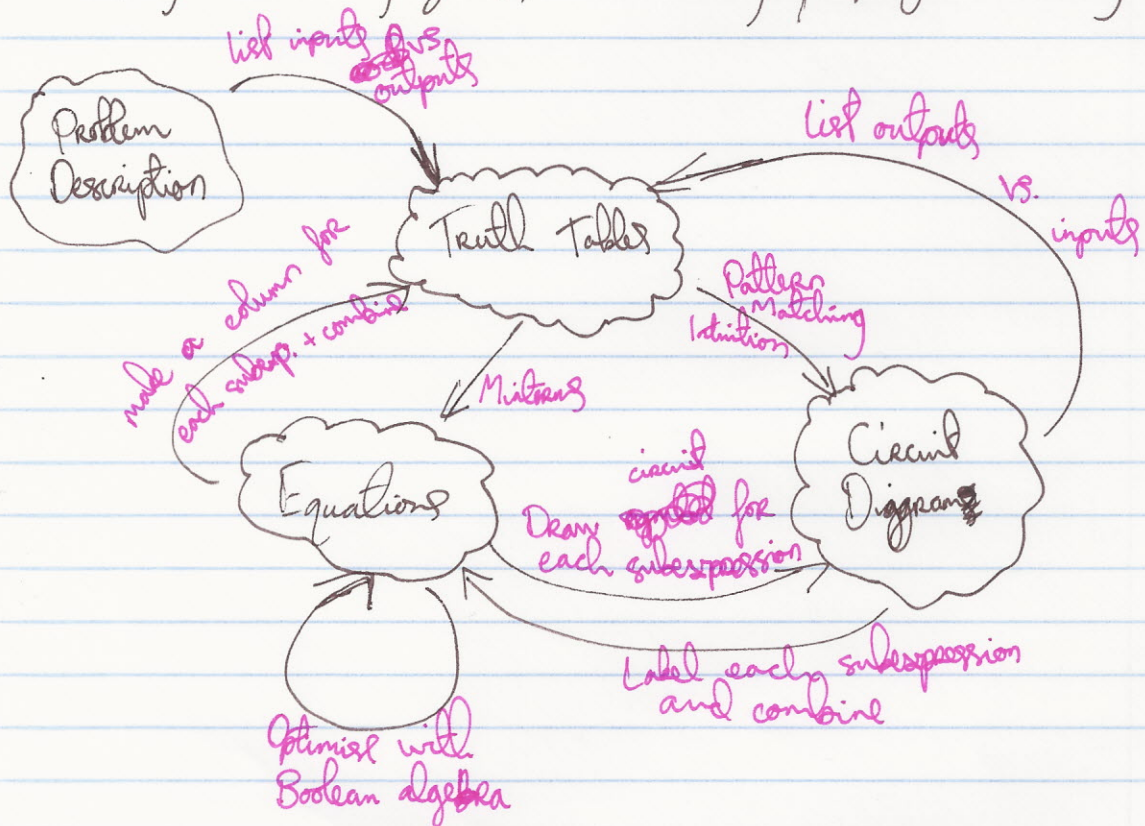


From Truth Tables to Circuit Diagrams (cont.)



This circuit looks different to the one we had before, but it does the same job. You could compare them in a number of ways to find which is better (e.g. number of gates, amount of propagation delay etc.).



This is where we are now.