

The Exam (cont.)

Question 2 (a) \rightarrow (c)

along these
lines

- 6 (a) Two's Complement ; Negation ; etc.
- 8 (b) Implementing expressions with 1 gate (either NAND or NOR)
- 6 (c) Create Subtraction ~~using~~ like we created a half-adder.

Question will say "half-subtractor".

0	1	0	1
0	0	1	1
0	1	1	0

\nwarrow This question is unfair he says, so that's why he's telling us this.

Question 3 (a) \rightarrow (d)

- 6 (a) Draw a circuit to implement ... and express as an equation.
This will be familiar.
- 6 (b) MAX
- 4 (c) MUX - The new thing today.
- 4 (d) Prove

Question 4 (a) \rightarrow (c)

- 8 (a) Given truth table get equation, simplify and implement
- 8 (b) Flip-flop and etc.
- 4 (c) Answer is six words long (~)